

## Class Assignment 04

Submitted on time? (YES/ NO): Yes

**Task 01:** Complete the Table 01.

**50 points**

**Task 02:** Attach screenshots of the simulated circuit of the experiment showing all Multimeter/  
simulation readings as mentioned in the class.

**30 points**

**Task -03:** Answer to the given question.

**20 points**

**Name & ID:** Md. Rifat Ahmed ~ 1931725042

---

### Task: 01

Table 4.1: Data for I - V characteristics

V (volts)	V <sub>R</sub> (volts)	V <sub>Z</sub> (volts)	I <sub>Z</sub> = V <sub>R</sub> / R (mA)
0.1	9.448 $\mu$ V	99.991 mV	19.999 nA
0.7	66.13 $\mu$ V	699.934 mV	139.988 nA
1.0	94.472 $\mu$ V	999.906 mV	199.984 nA
3.0	283.414 $\mu$ V	3 V	599.965 nA
5.0	92.521 mV	4.907 V	196.848 $\mu$ A
6.0	1.044 V	4.956 V	2.221 mA
10.0	5.013 V	4.987 V	10.665 mA

Table 4.2: Data for Load Regulation

POT_R (k ohm)	V <sub>220</sub> (mV)	V <sub>L</sub> (volts)	I <sub>L</sub> (Amp)= V <sub>220</sub> /220
1 k	897.643 mV	4.978 V	4.08 mA
3 k	340.542 mV	4.984 V	1.548 mA
5k	210.119 mV	4.986 V	955.092 $\mu$ A
9k	118.981 mV	4.986 V	540.828 $\mu$ A
10k	107.341 mV	4.986 V	487.92 $\mu$ A

Table 4.3: Data for Line Regulation.

V (volts)	V <sub>L</sub> (volts)
1.0	721.844 mV
3.0	2.166 V
6.0	4.331 V
9.0	4.97 V
10.0	4.978 V
11.0	4.983 V
12.0	4.988 V

**Task: 02**

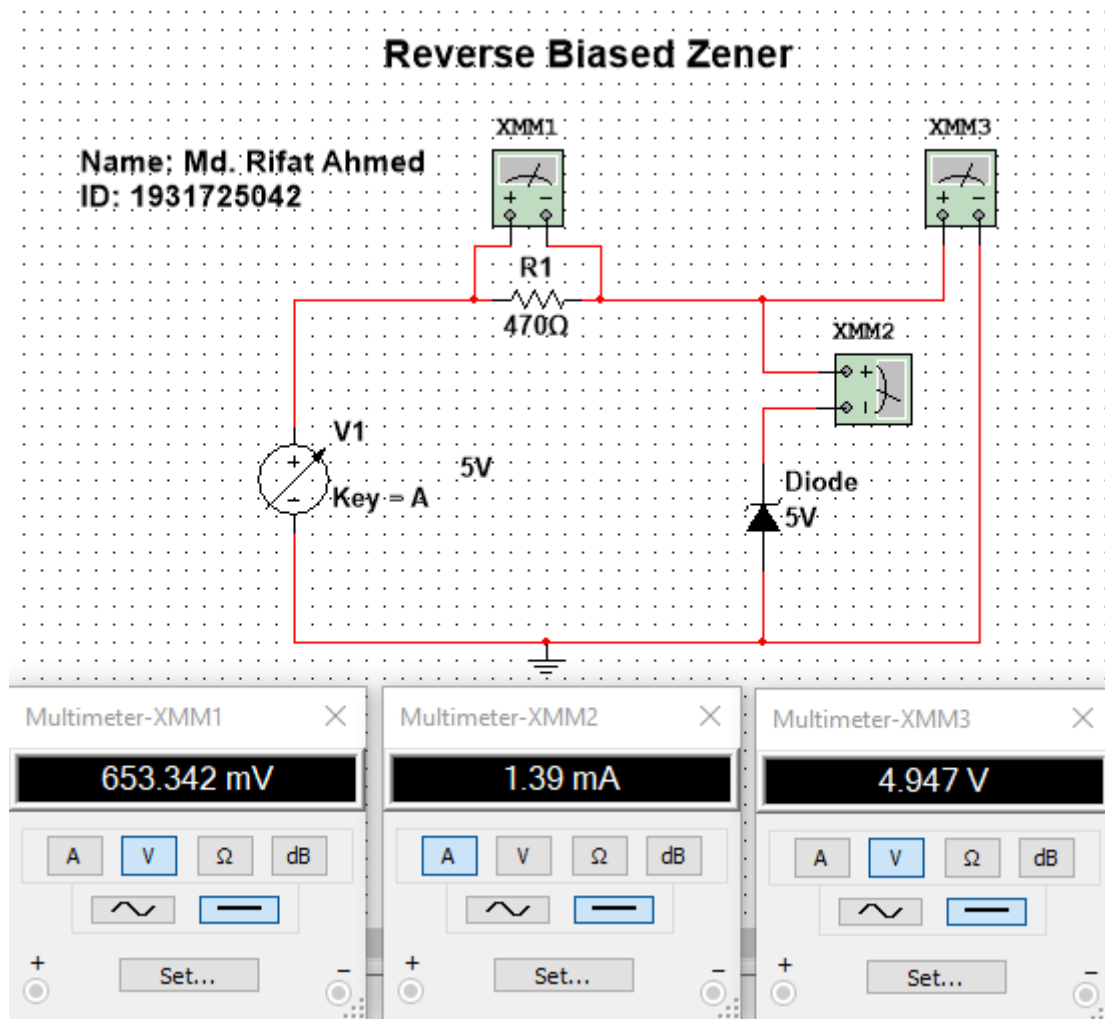


Figure 1: Reverse Biased Zener Circuit

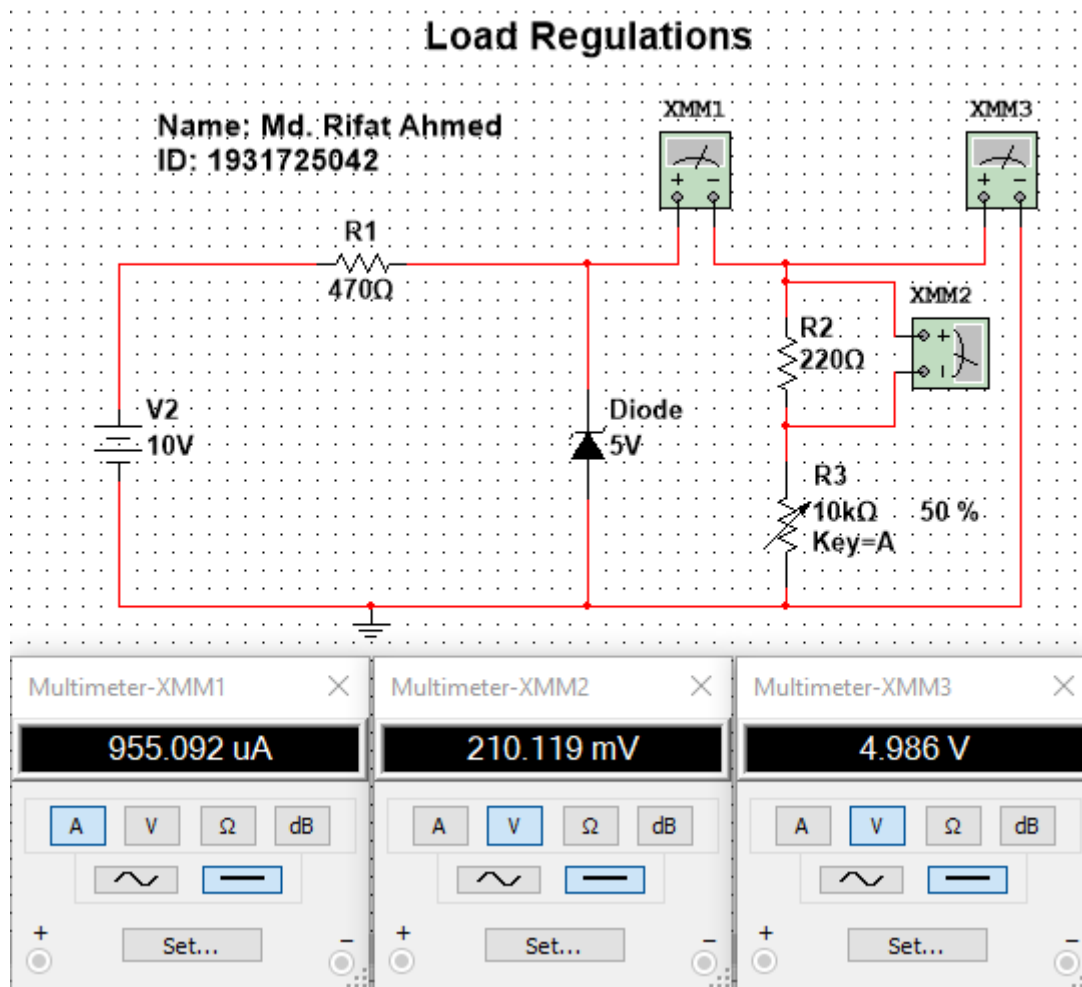


Figure 2: Load Regulations Circuit

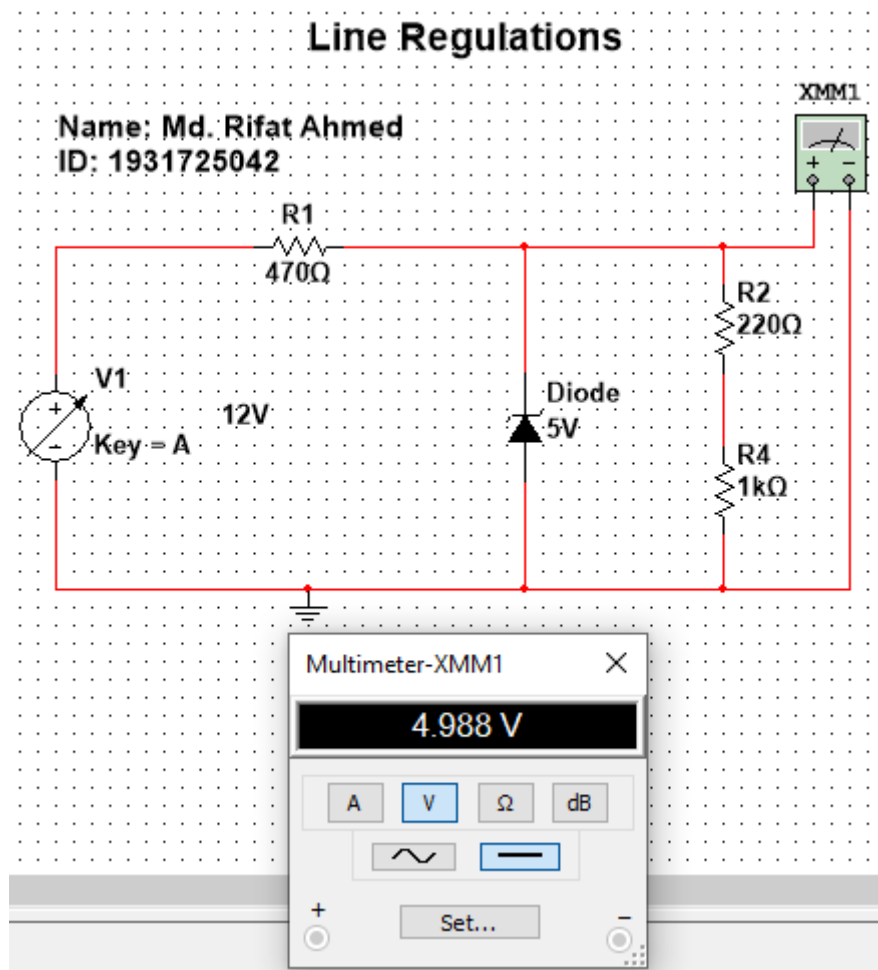


Figure 3: Line Regulations Circuit

## Class Assignment 04

### **Task: 03**

#### **1. What is the difference between a Zener Diode and a diode?**

**Ans:** A normal diode only conducts in the forward bias region and does not conduct when reverse biased because they might be damaged if they're reverse biased. But on the other hand, a Zener diode can conduct in three regions: forward, leakage and breakdown. In forward bias region it acts like a normal silicon diode, in the leakage region it can conduct a small amount of reverse saturation current and in the breakdown region it works for a fixed amount of voltage.

#### **2. What is called a Zener Voltage?**

**Ans:** The voltage that causes a diode to enter the Zener region in the negative bias region is called Zener voltage ( $V_Z$ ).