

Quiz 01

ANSWER ALL THE QUESTION
Total Marks: 20 (Time: 35 Minutes)

N.B.: Don't forget to use correct unit!

1. In the lab experiments we examined different types of rectifier circuits. 7 pt
 - a. How many types of rectifier circuits are there? Name them. 3
 - b. Why did we use capacitor in parallel with the load resistor? 2
 - c. Between the capacitors of values $0.22 \mu\text{F}$ and $10 \mu\text{F}$ which one was more preferable? 2

2. Consider the circuit of figure A. 7 pts
 - a. What is the name of the circuit of the output waveforms of figure-1.b? 2
 - b. Write the name of all equipments clearly to construct and implement the circuits of **(a & b)** given below. 5

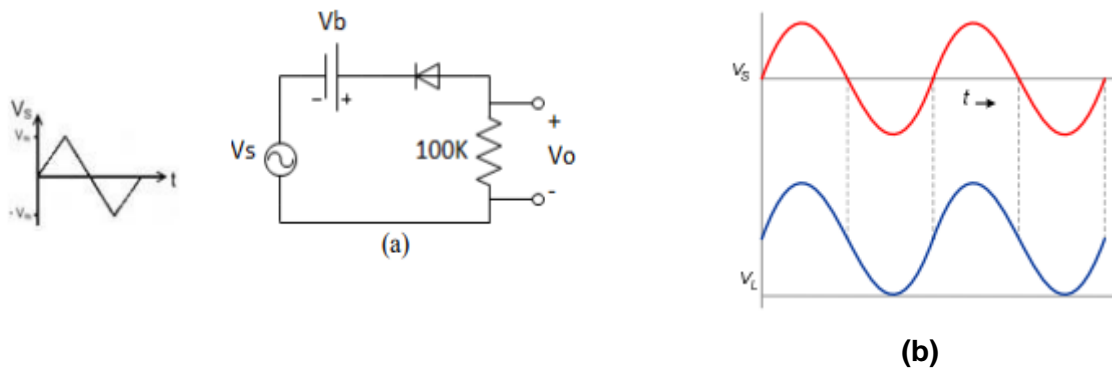


Figure: 01

3. In the lab experiments we used two types of diode. 3 pts
 - a. In the study of I-V characteristics of diode, how did you find Q-point? 1
 - b. While studying Diode 02, how did you test that it acts as a voltage regulator? 2
 - c. From the experiments explain how is **Diode -01** different from a **Diode-02**? 2

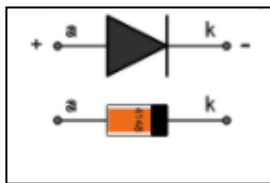


Figure 02: **Diode -01**

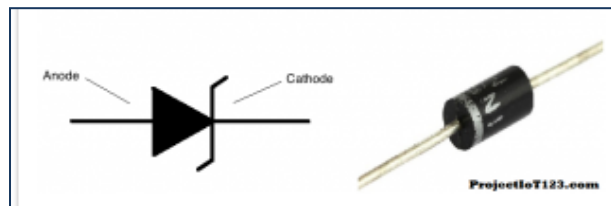


Figure 02: **Diode- 02**

4. Choose/ write the best answer.

- i. DC power must should be connected to forward bias as follows:
 - A. +anode, -cathode
 - B. +cathode, - anode
 - C. +anode, +cathode
 - D. -anode, -cathode
- ii. *Providing a constant output regardless of ac input or load resistance changes is the function of a:*
 - A. *Filter*
 - B. *Transformer*
 - C. *Rectifier*
 - D. *Regulator*
- iii. *If the frequency of the applied ac signal to a half wave rectifier is 100 Hz, the frequency of the pulsating dc output would be*
 - A. 25 Hz
 - B. 50Hz
 - C. 100 Hz
 - D. 120 Hz
- iv. *Ideally the voltage drop across a conducting diode is*
- v. *Zener diodes allow a current to flow in the reverse direction, when the volatge reaches to above a certain value. (True/ False)*
- vi. *When reverse breakdown occurs in a diode –*
 - A. *Voltage increases & current is constant*
 - B. *Voltage and current increase exponentially*
 - C. *Voltage is constant & current increases*
 - D. *No change happens*