

Name: Md. Ritab Ahmed

ID: 1931725042

Course: EEE111L

Section: 7

Quiz

Answer to the Question No-1

a) There are two types of rectifier circuits.

1) Half-wave rectifier

2) Full-wave rectifier

b) Using the capacitor in parallel with load resistor reduces the ripple in the output voltage giving us a much smoother curve..

c) Between the capacitor of values $0.22\mu\text{F}$ and $10\mu\text{F}$ the $10\mu\text{F}$ was more preferable because it gave us a more DC like output curve.

Answer to the Question No-2

a) The name of the circuit of the output wave-forms of figure-1(b) is the parallel clipper circuit.

b) The name of the equipments needed to construct a & b circuits are:

- * Diode
- * Resistor
- * DC Power source
- * Trainer Board
- * Signal Generator
- * Digital Multimeter
- * Oscilloscope
- * Wires as required

Answer to the Question No-3

- a) The point where the load line crosses with the output curve is the Q-point.
- b) Diode D_2 is a Zener diode and while doing the experiment we saw the V_Z increasing gradually along with input voltage.
- c) Diode 1 is a general diode which only works in forward biased condition.
- Diode 2 is a Zener diode that works in both forward and reverse biased condition. But in a reverse biased it only works after reaching a certain point of voltage which is Zener voltage.

Name: Md. Ribat Ahmed

ID: 1931725042 | Section: 7

Answer to the Question No - 4

- i) A) + anode , - cathode
- ii) D) Regulator
- iii) ~~B) 50 Hz~~ C) 100HZ
- iv) 0 volts but for silicon diode 0.7 Volts.
- v) True
- vi) B) ~~Voltage and current increases exponentially~~
C) Voltage is constant & current increases