


**North South University**  
**Department of Electrical and Computer Engineering**  
**EEE/ETE 111L**  
**Fall 2021**

**Quiz 02**

ANSWER ALL THE QUESTION  
 Total Marks: 25 (Time: 30 Minutes)


N.B.: Write each formula clearly. Don't forget to use correct unit!

1. The characteristics of a BJT transistor are measured by two characteristics curve (Figure: A) 6 pts
  - i. Write the name of the two curves given below. 2
  - ii. What are the name of the variables, a, b, x, y, z in the curves given below? 2.5
  - iii. What is the function of a BJT? 1.5

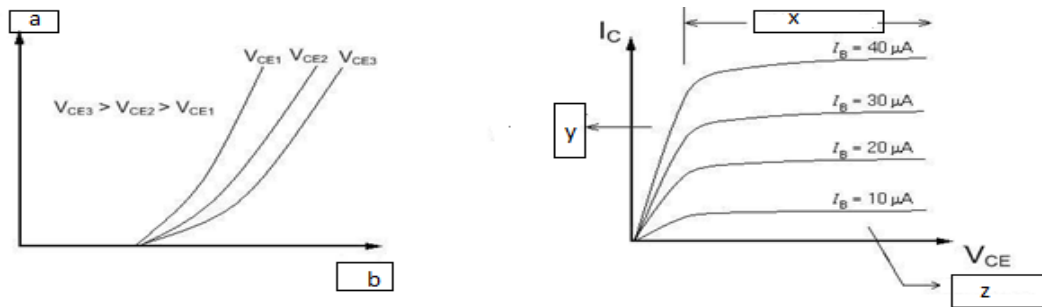

**Figure: A**

2. Consider the circuit of Figure B. 8 pts
  - a. What do you understand by "Biasing a BJT circuit"? 2
  - b. What are the names of the circuits (Fig. B)? 2
  - c. Draw the symbol of the transistor used in the circuit with proper labelling. 1
  - d. During the lab experiment which circuit showed better stability? 1
  - e. Mention TWO differences between BJT and MOSFET you observed during experiment. 2

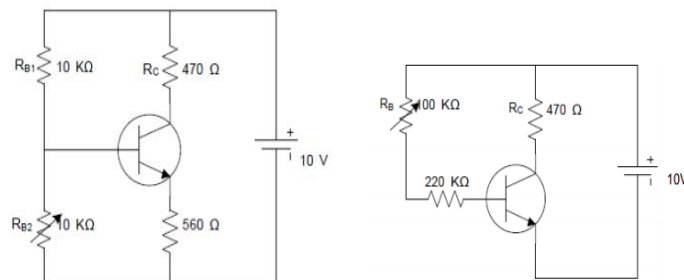

**Figure: B**

3. What is the name of the equipment of given below? What are the function of A, D, and E? (A → cursor, D → Volt/Div, E → Sec/Div) 4 pts  
1+3

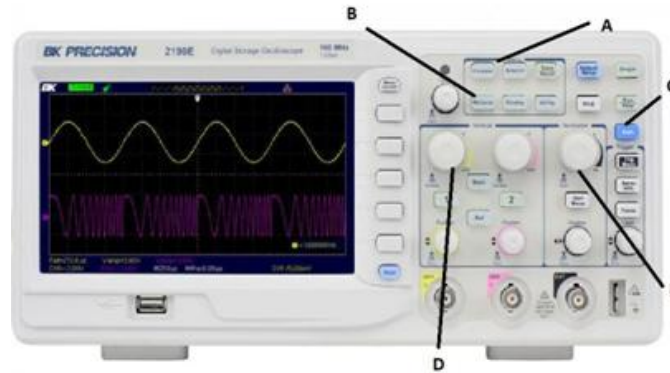


Figure: C

4. What is the name of the graph given below? From the experiment explain how does a MOSFET work in the three working region mentioned in the graph? 3 pts  
1+2

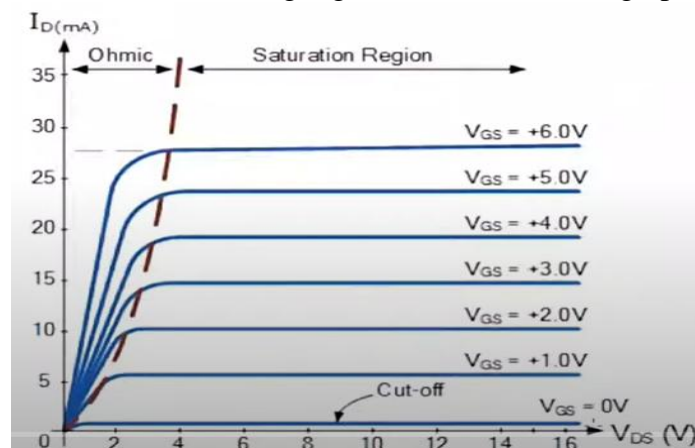


Figure: D

5. **True/ false and Fill in the blanks:** 4 pts  
1
- When forward biased voltage is applied to the p-n junction diode, the width of depletion region decreases. ( ) 1
  - BJT is a current controlled device whereas MOSFET is a voltage controlled device. ( ) 1
  - Zener diode permits current to flow in the (i) ..... direction as normal diode, but will also allow it to flow in the reverse direction when the voltage is above a certain value of the breakdown voltage known as the (ii) ..... voltage. 2