

Set: Believe in yourself, don't cheat

Name: Md. Rifat Ahmed

ID: 1931725042

Section: 7

Set: 3

Part 1:

Construct the following circuit in Multisim where, $V_s = 10$ (variable), diode is *virtual* and resistances are $470\ \Omega$, $220\ \Omega$ and $1\ \text{k}\Omega$.

Measure the value of load voltage V_L and complete the table 01.

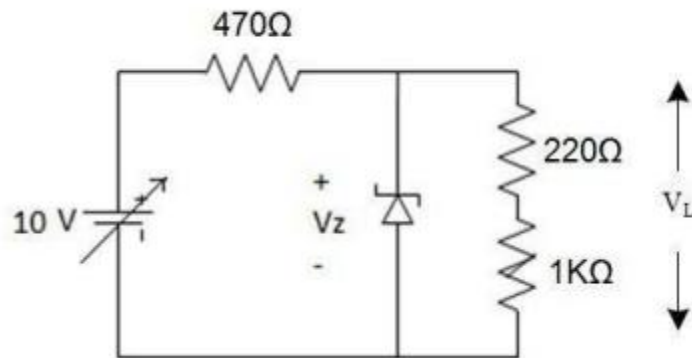


Table 01

V (volts)	V_L (volts)
1.0	721.844 mV
3.0	2.166 V
6.0	4.331 V
8.0	4.958 V
11.0	4.983 V
12.0	4.988 V
16.0	4.999 V

Part 02:

Attach the screenshots of the constructed circuit during the measurement of V_L when $V_s = 16$ V. (below)

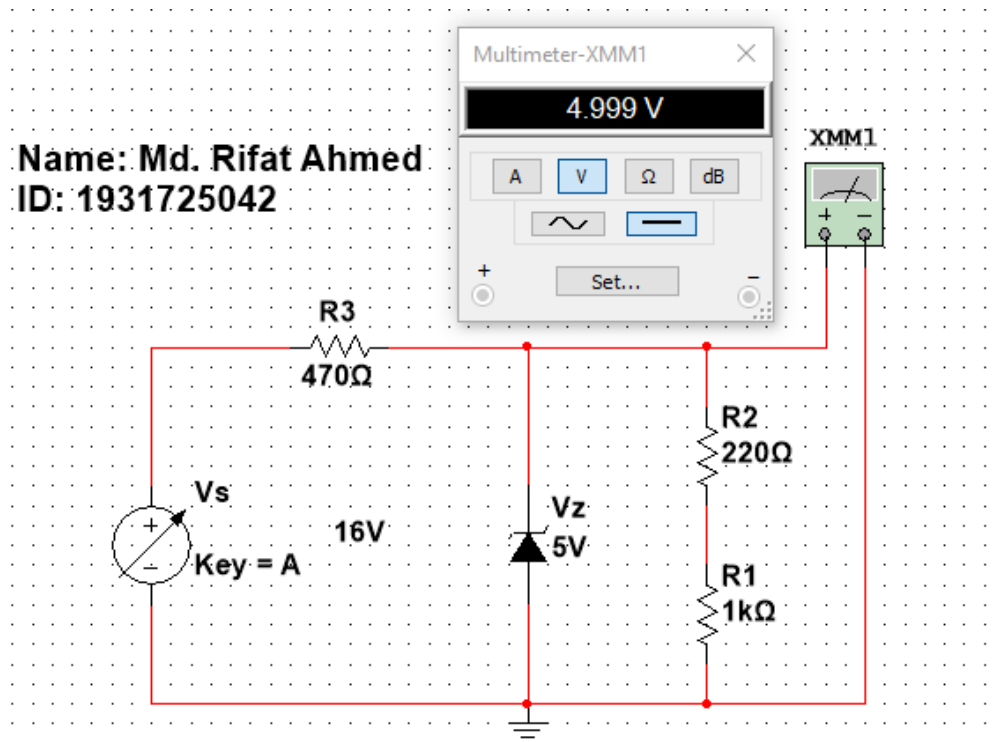


Figure – Circuit when $V_s = 16$ V

Part 03:

Answer the following questions in your own words.

1. What is the name of the experiment?
Ans: Zener Diode Applications (Load Regulation)
2. What happens to the load voltage when V_s increases? And why?
Ans: When V_s increases the Load voltage also increases but the virtual diode used here is 5V so when more than 5V is applied in the V_s the voltage across the load is still close to 5V and cannot cross it as in reverse bias the Zener diode only lets a fixed amount of Voltage pass through it so through the load the same amount will pass.
3. What is the name and code of this 1 credit course?
Ans: Analog Electronics Lab (EEE111L)
4. What is the function of the diode used in this circuit?
Ans: The function of Zener diode used in this circuit is Regulating Load.
5. What was the Zener voltage rating we used in the lab?
Ans: 5V